

# **DC MOTOR DRIVES (MEP 1422)**

**Dr. Nik Rumzi Nik Idris**  
**Department of Energy Conversion**  
**FKE, UTM**

# Contents

- **Introduction**
  - Trends in DC drives
  - DC motors
- **Modeling of Converters and DC motor**
  - Phase-controlled Rectifier
  - DC-DC converter (Switch-mode)
  - Modeling of DC motor
- **Closed-loop speed control**
  - Cascade Control Structure
  - Closed-loop speed control - an example
    - Torque loop
    - Speed loop
- **Summary**

# INTRODUCTION

- DC DRIVES: Electric drives that use DC motors as the prime movers
- DC motor: industry workhorse for decades
- Dominates variable speed applications before PE converters were introduced
- Will AC drive replaces DC drive ?
  - Predicted 30 years ago
  - DC strong presence – easy control – huge numbers
  - AC will eventually replace DC – at a slow rate

# Introduction

## DC Motors


- Advantage: Precise torque and speed control without sophisticated electronics
- Several limitations:
  - Regular Maintenance
  - Heavy
  - Sparking
  - Expensive
  - Speed limitations

# Introduction

## DC Motors

Stator: field windings

Rotor: armature windings

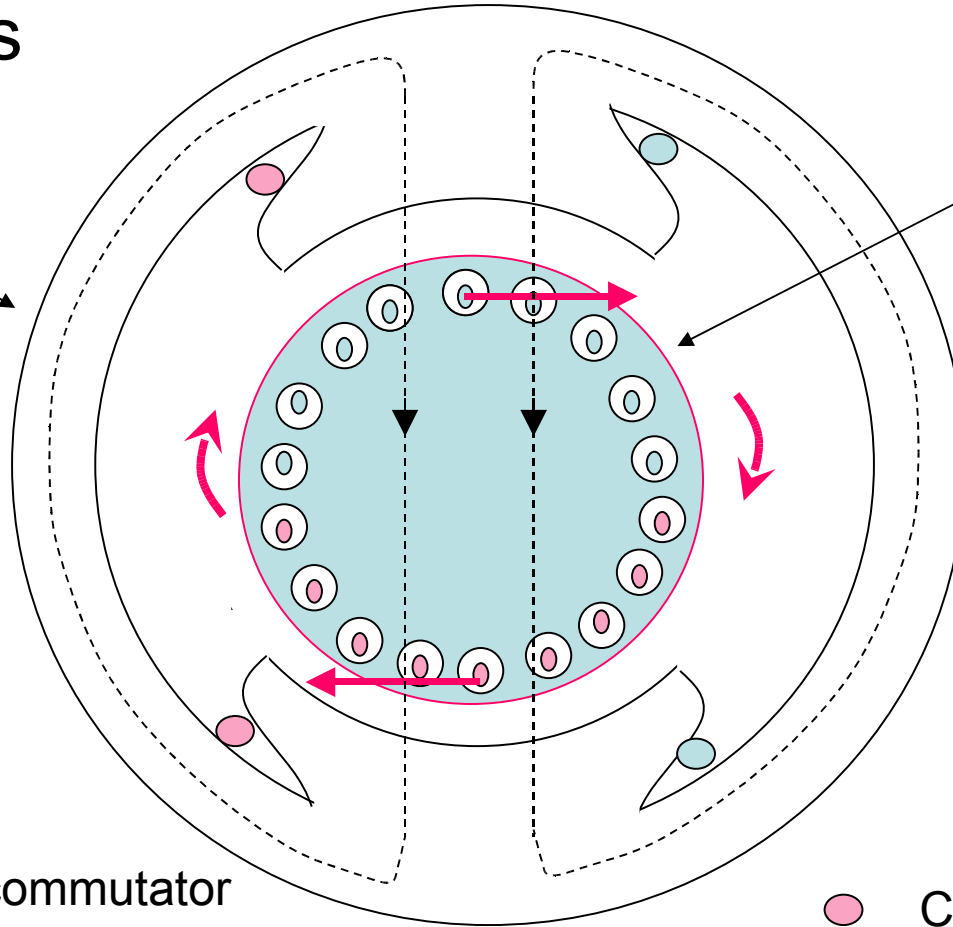


- Mechanical commutator

- Large machine employs compensation windings

● Current in

● Current out

# Introduction

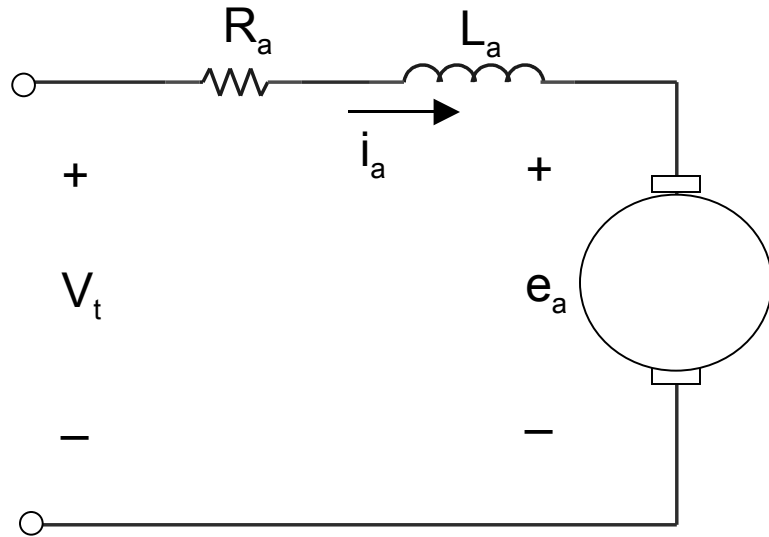


$$v_t = R_a i_a + L \frac{di_a}{dt} + e_a$$

$$T_e = k_t \phi i_a$$

Electric torque

$$e_a = k_E \phi \omega$$

Armature back e.m.f.

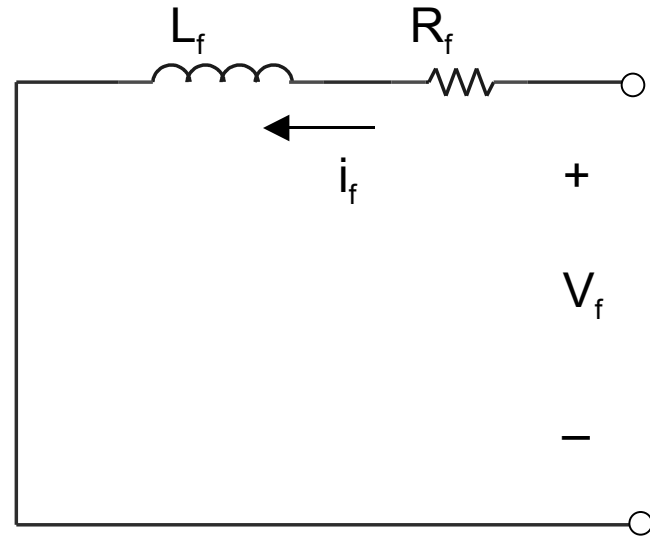

$$v_f = R_f i_f + L \frac{di_f}{dt}$$

## Introduction

Armature circuit:

$$V_t = R_a i_a + L \frac{di_a}{dt} + e_a$$

In steady state,

$$V_t = R_a I_a + E_a$$

Therefore speed is given by,

$$\omega = \frac{V_t}{k_T \phi} - \frac{R_a T_e}{(k_T \phi)^2}$$

Three possible methods of speed control:

Field flux

Armature voltage  $V_t$

Armature resistance  $R_a$


## Introduction

Armature voltage control : retain maximum torque capability

Field flux control (i.e. flux reduced) : reduce maximum torque capability

For wide range of speed control

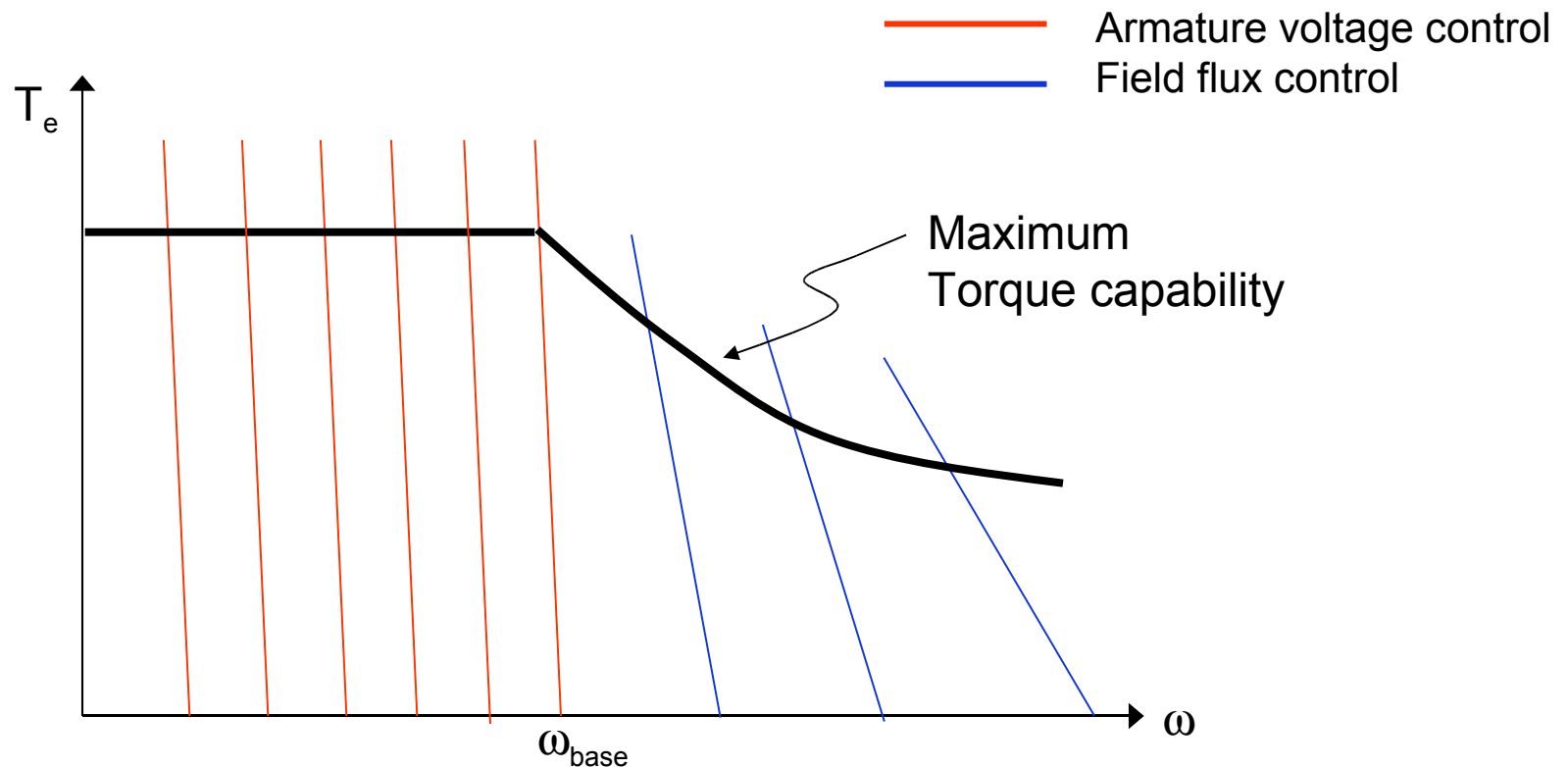0 to  $\omega_{\text{base}}$   $\rightarrow$  armature voltage control, above  $\omega_{\text{base}}$   $\rightarrow$  field flux reduction





# MODELING OF CONVERTERS AND DC MOTOR


## POWER ELECTRONICS CONVERTERS

Used to obtain variable armature voltage

- Efficient  
Ideal : lossless
- Phase-controlled rectifiers (AC  $\rightarrow$  DC)
- DC-DC switch-mode converters(DC  $\rightarrow$  DC)



# Modeling of Converters and DC motor

## Phase-controlled rectifier (AC–DC)

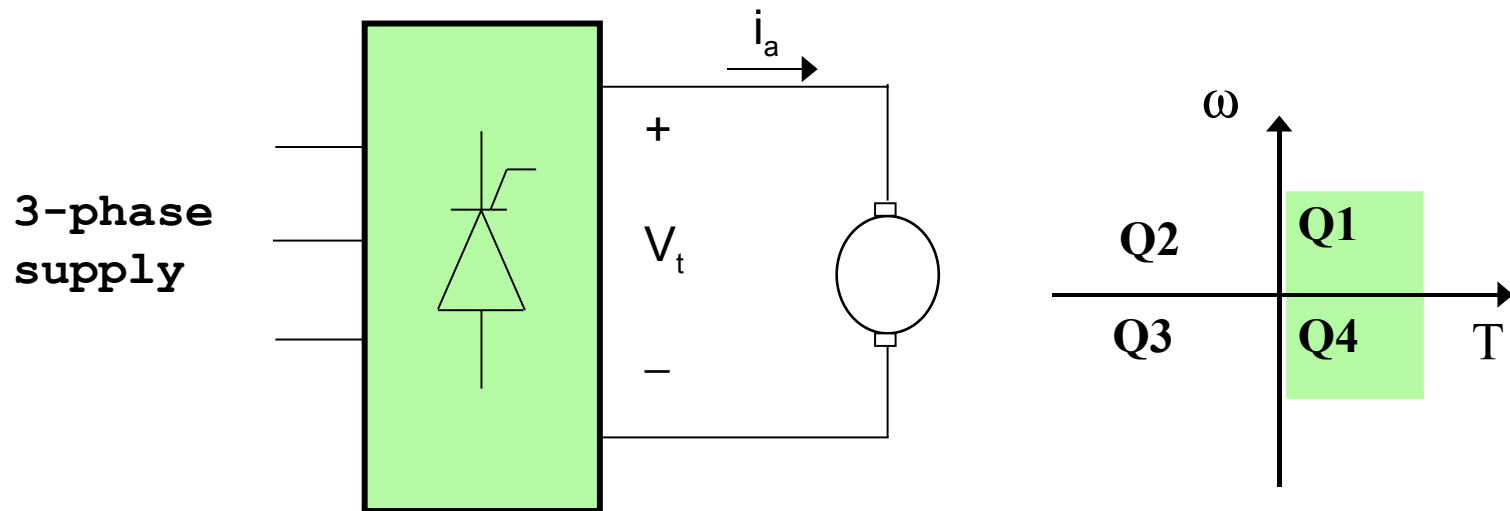



# Modeling of Converters and DC motor

## Phase-controlled rectifier

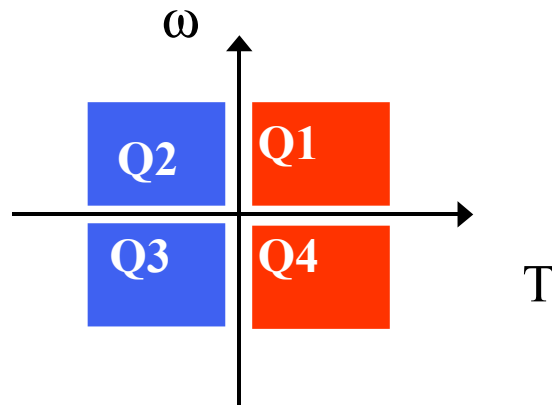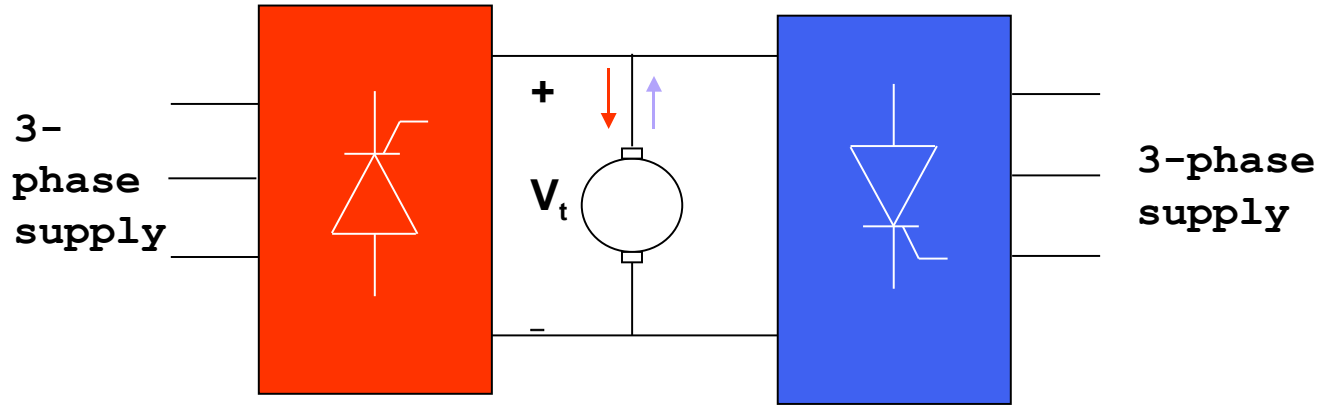

# Modeling of Converters and DC motor


## Phase-controlled rectifier

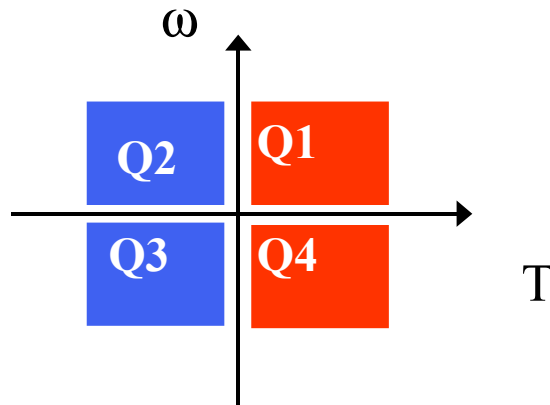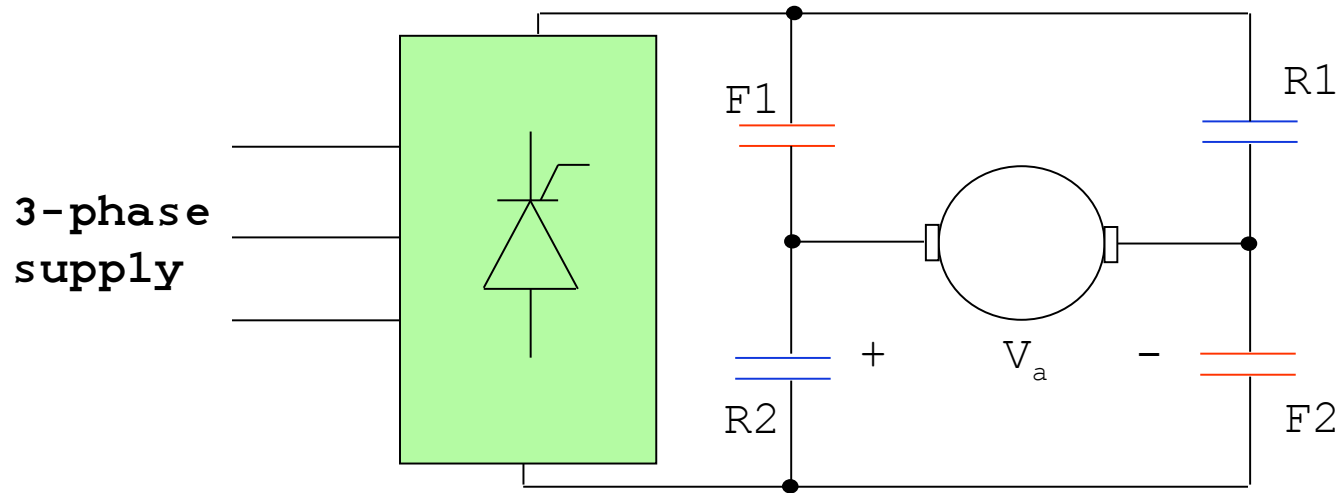

## Modeling of Converters and DC motor
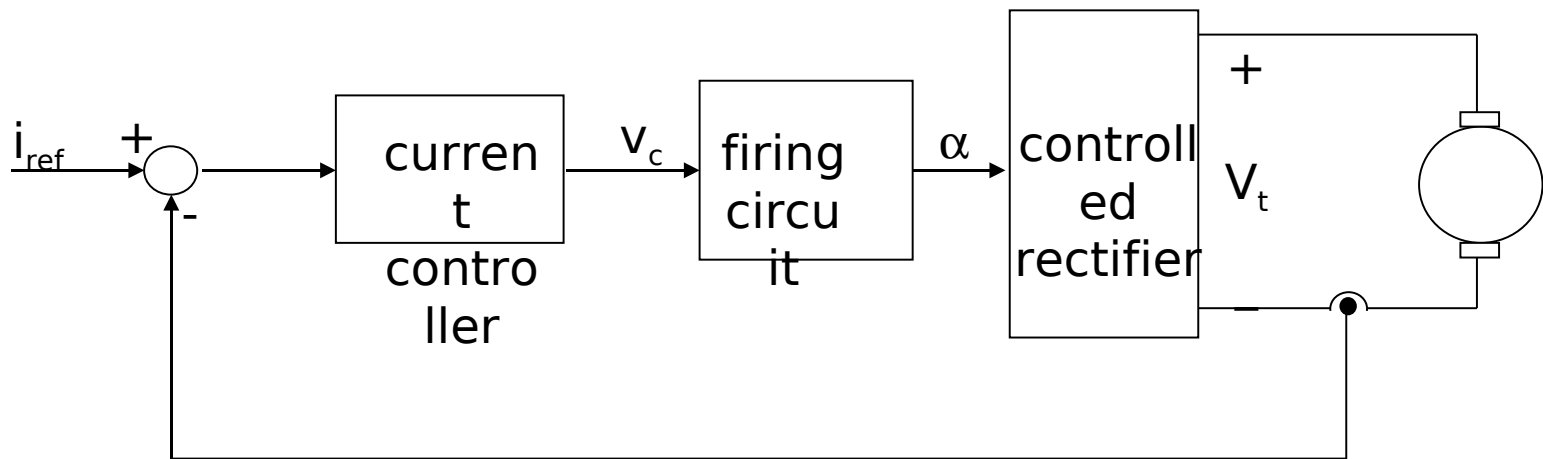
### Phase-controlled rectifier (continuous current)


- Firing circuit –firing angle control
  - Establish relation between  $v_c$  and  $V_t$



# Modeling of Converters and DC motor

## Phase-controlled rectifier (continuous current)

- Firing angle control

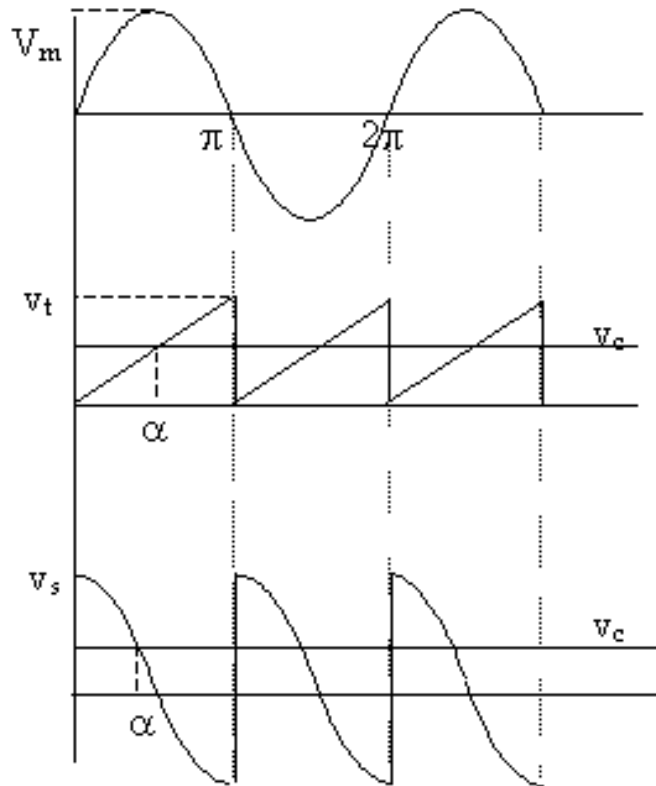

linear firing angle control

$$\frac{V_t}{180} = \frac{V_c}{\alpha} \quad \alpha = \frac{V_c}{V_t} 180$$

$$V_a = \frac{V_m}{\pi} \cos\left(\frac{V_c}{V_t} 180\right)$$

Cosine-wave crossing control


$$V_c = V_s \cos \alpha$$

$$V_a = \frac{V_m}{\pi} \frac{V_c}{V_s}$$

## Modeling of Converters and DC motor
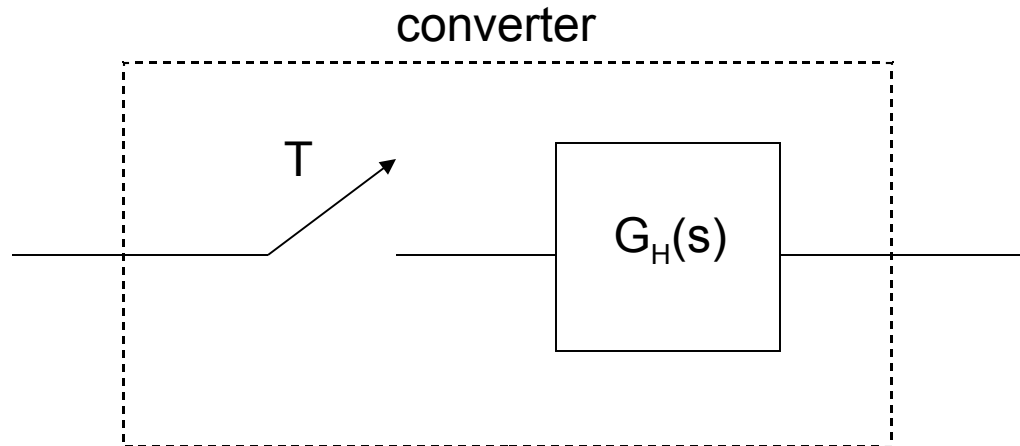
### Phase-controlled rectifier (continuous current)


- Steady state: linear gain amplifier
  - Cosine wave-crossing method
- Transient: sampler with zero order hold



- $T$  – 10 ms for 1-phase 50 Hz system
- 3.33 ms for 3-phase 50 Hz system

# Modeling of Converters and DC motor
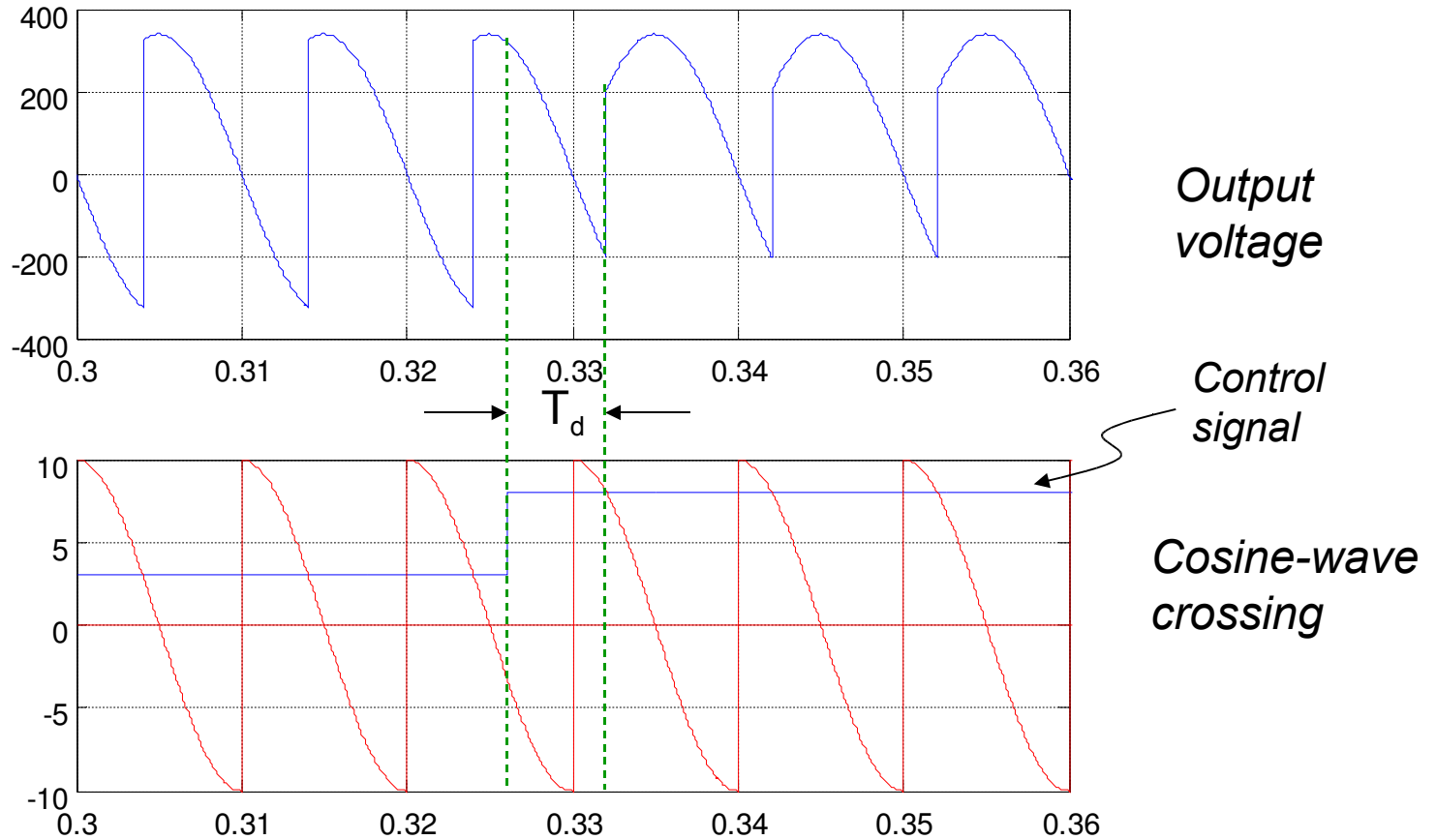
## Phase-controlled rectifier (continuous current)



$T_d$  – Delay in average output voltage generation  
0 – 10 ms for 50 Hz single phase system





## Modeling of Converters and DC motor

### Phase-controlled rectifier (continuous current)

- Model simplified to linear gain if bandwidth (e.g. current loop) much lower than sampling frequency
  - ⇒ Low bandwidth – limited applications
- Low frequency voltage ripple → high current ripple → undesirable



# Modeling of Converters and DC motor

## Switch-mode converters

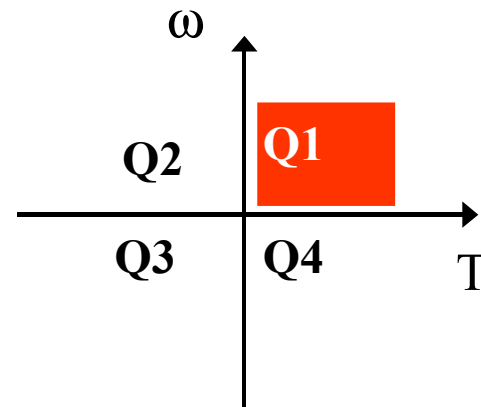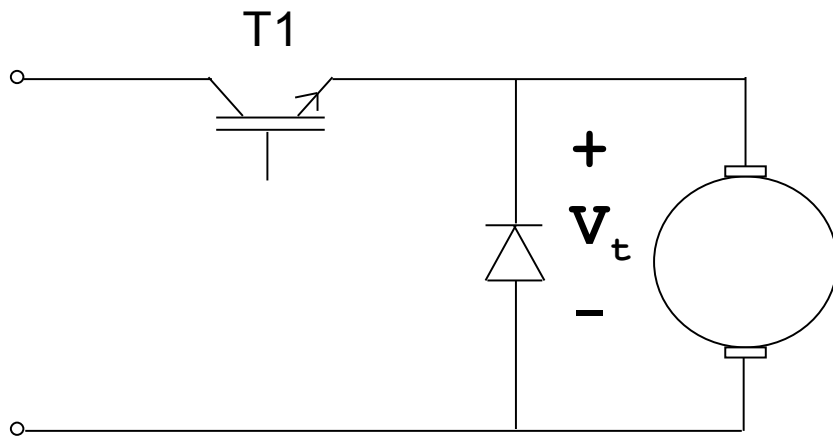

# Modeling of Converters and DC motor

## Switch-mode converters

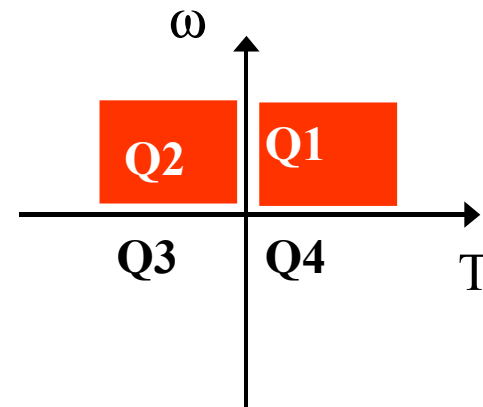
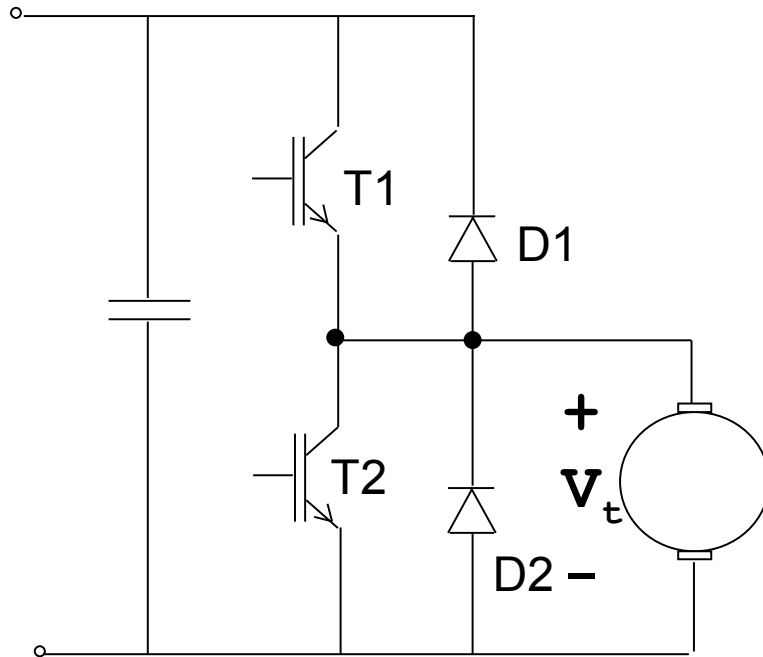


Q1  $\rightarrow$  T1 and D2

Q2  $\rightarrow$  D1 and T2

# Modeling of Converters and DC motor

## Switch-mode converters

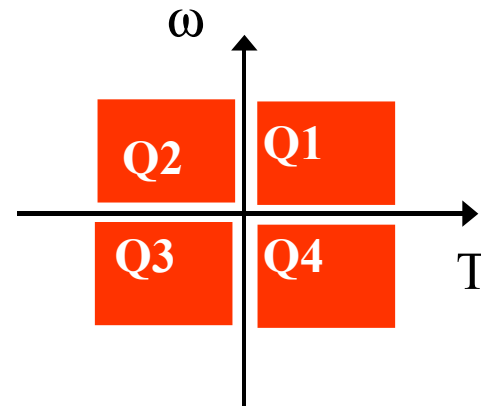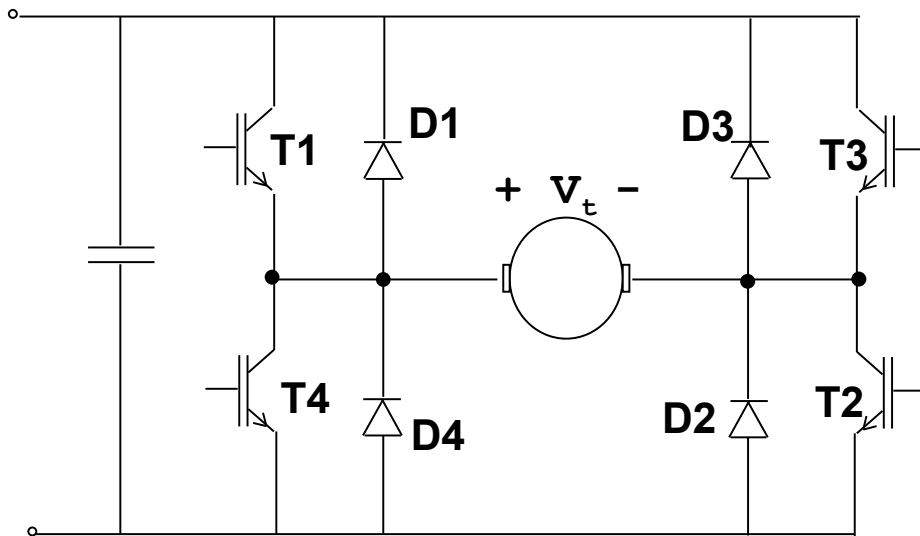


# Modeling of Converters and DC motor

## Switch–mode converters

- Switching at high frequency
  - Reduces current ripple
  - Increases control bandwidth
- Suitable for high performance applications



# Modeling of Converters and DC motor

## Switch-mode converters - modeling

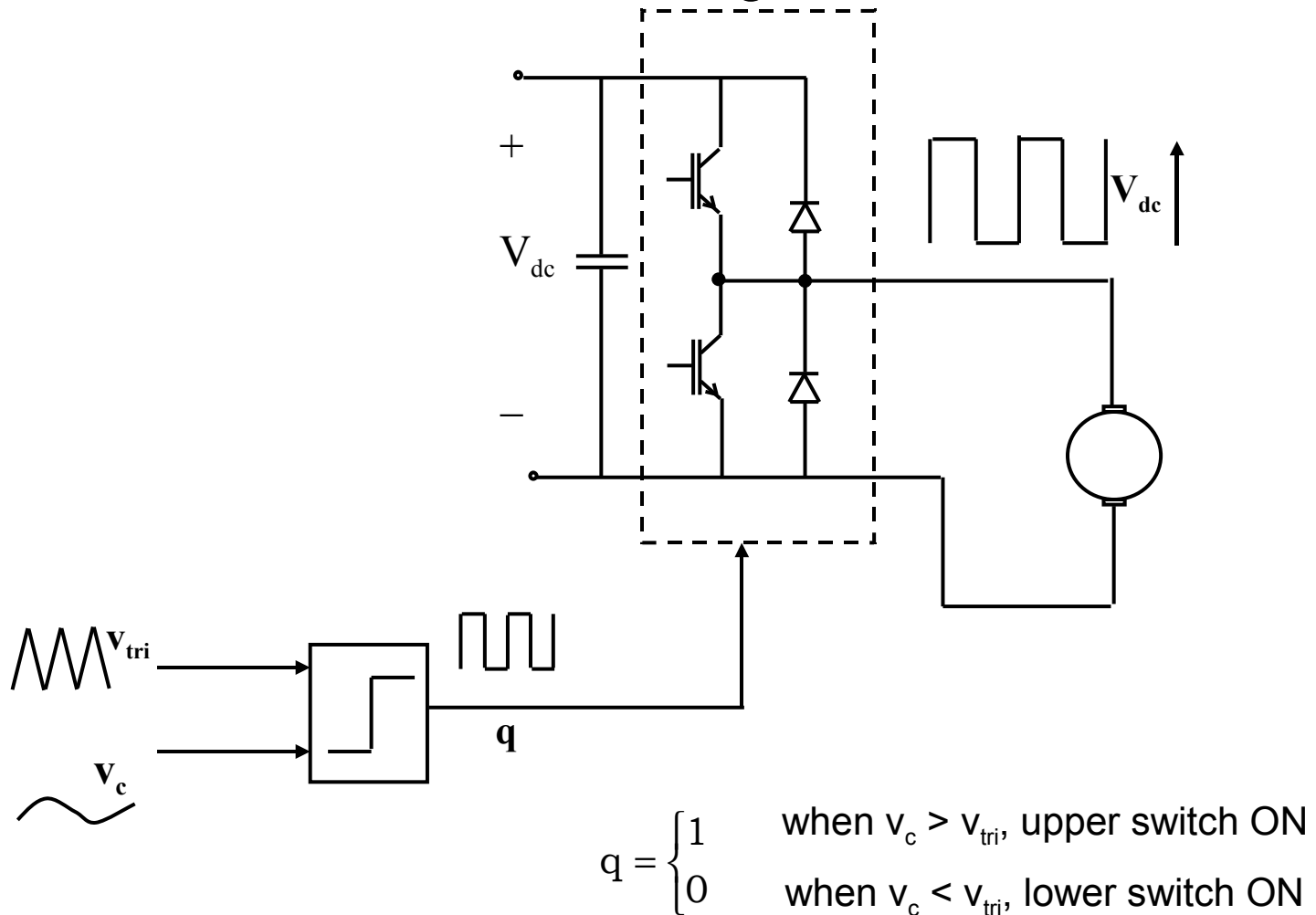


# Modeling of Converters and DC motor
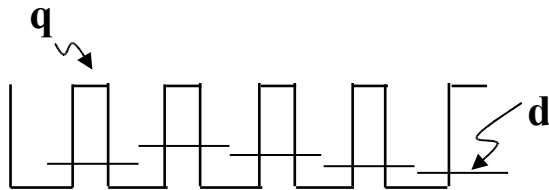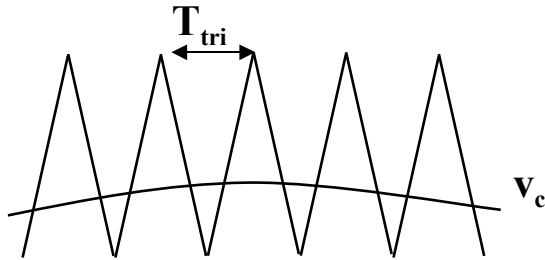
## Switch-mode converters – averaged model



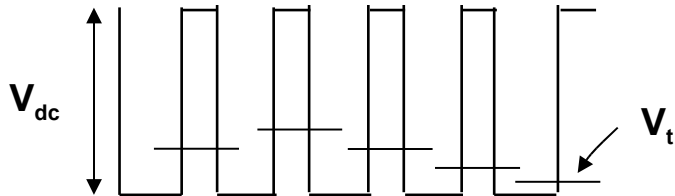
$$d = \frac{1}{T_{tri}} \int_t^{t+T_{tri}} q dt = \frac{t_{on}}{T_{tri}}$$



$$V_t = \frac{1}{T_{tri}} \int_0^{dT_{tri}} v_{dc} dt = dV_{dc}$$

## Modeling of Converters and DC motor
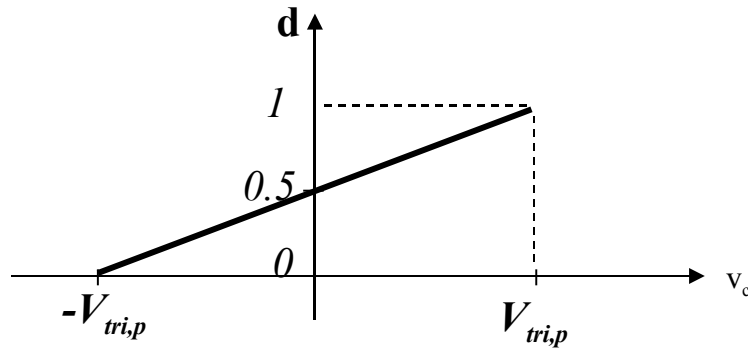
### Switch-mode converters – averaged model



$$d = 0.5 + \frac{v_c}{2V_{tri,p}}$$

$$V_t = 0.5V_{dc} + \frac{V_{dc}}{2V_{tri,p}} v_c$$



# Modeling of Converters and DC motor

## DC motor – small signal model

$$v_t = i_a R_a + L_a \frac{di_a}{dt} + e_a$$

$$T_e = T_l + J \frac{d\omega_m}{dt}$$

$$T_e = k_t i_a$$

$$e_e = k_t \omega$$

Extract the dc and ac components by introducing small perturbations in  $V_t$ ,  $i_a$ ,  $e_a$ ,  $T_e$ ,  $T_L$  and  $\omega_m$

ac components

$$\tilde{v}_t = \tilde{i}_a R_a + L_a \frac{d\tilde{i}_a}{dt} + \tilde{e}_a$$

$$\tilde{T}_e = k_E (\tilde{i}_a)$$

$$\tilde{e}_e = k_E (\tilde{\omega})$$

$$\tilde{T}_e = \tilde{T}_L + B\tilde{\omega} + J \frac{d(\tilde{\omega})}{dt}$$

dc components

$$V_t = I_a R_a + E_a$$

$$T_e = k_E I_a$$

$$E_e = k_E \omega$$

$$T_e = T_L + B(\omega)$$

# Modeling of Converters and DC motor

## DC motor – small signal model

Perform Laplace Transformation on ac components

$$\tilde{v}_t = \tilde{i}_a R_a + L_a \frac{d\tilde{i}_a}{dt} + \tilde{e}_a \quad \longrightarrow \quad V_t(s) = I_a(s)R_a + L_a s I_a + E_a(s)$$


$$\tilde{T}_e = k_E (\tilde{i}_a) \quad \longrightarrow \quad T_e(s) = k_E I_a(s)$$

$$\tilde{e}_e = k_E (\tilde{\omega}) \quad \longrightarrow \quad E_a(s) = k_E \omega(s)$$

$$\tilde{T}_e = \tilde{T}_L + B\tilde{\omega} + J \frac{d(\tilde{\omega})}{dt} \quad \longrightarrow \quad T_e(s) = T_L(s) + B\omega(s) + sJ\omega(s)$$


# Modeling of Converters and DC motor

## DC motor – small signal model

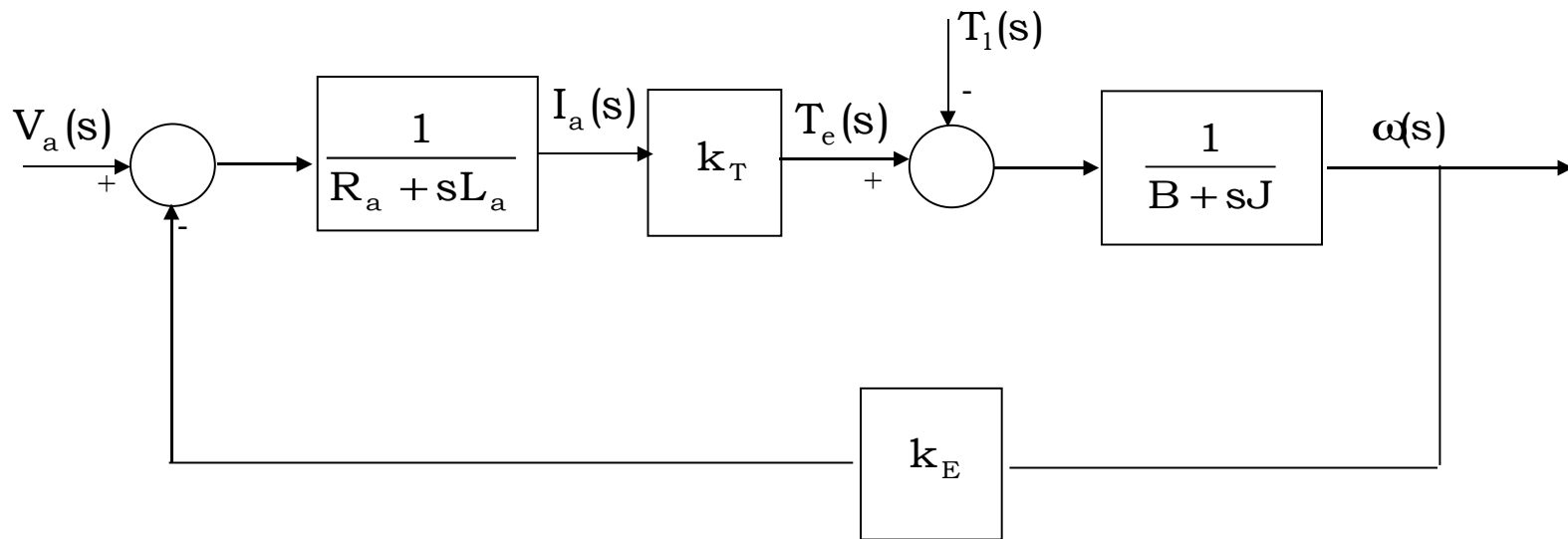

# CLOSED-LOOP SPEED CONTROL

## Cascade control structure

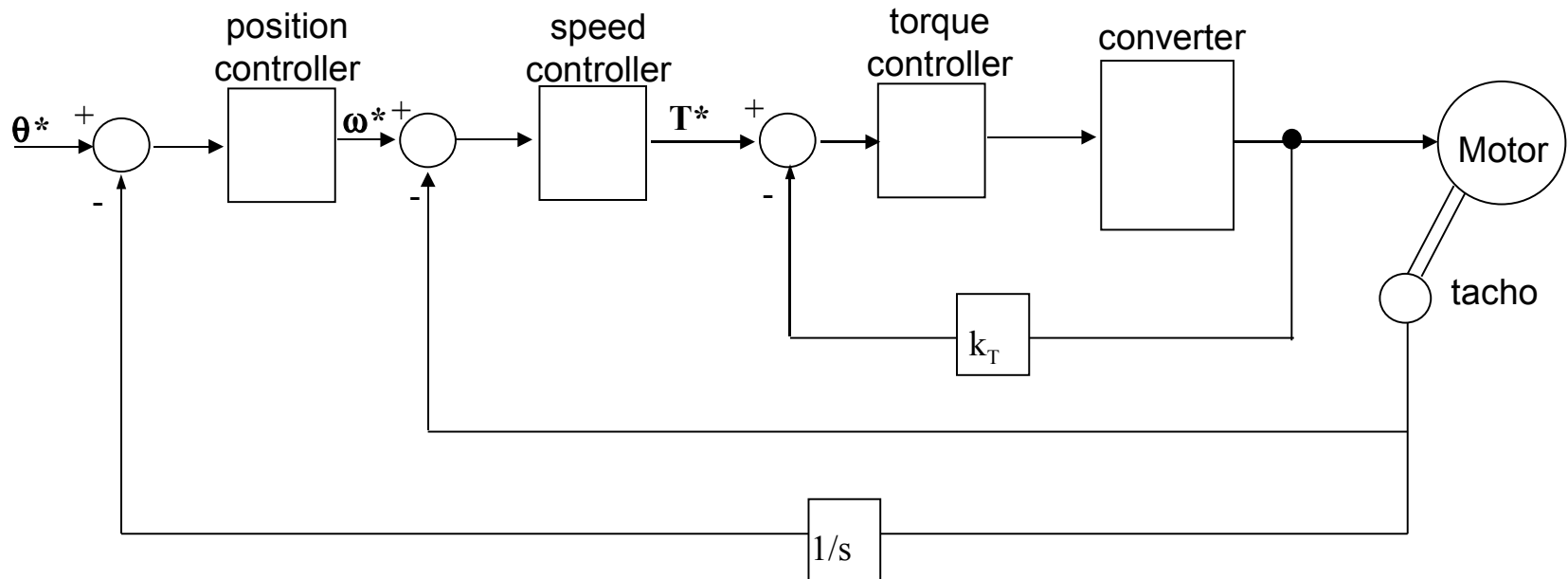

- The control variable of inner loop (e.g. torque) can be limited by limiting its reference value
- It is flexible – outer loop can be readily added or removed depending on the control requirements

## CLOSED-LOOP SPEED CONTROL

### Design procedure in cascade control structure

- Inner loop (current or torque loop) the fastest – largest bandwidth
- The outer most loop (position loop) the slowest – smallest bandwidth
- Design starts from torque loop proceed towards outer loops

## CLOSED-LOOP SPEED CONTROL

### Closed-loop speed control – an example

#### OBJECTIVES:

- Fast response – large bandwidth
- Minimum overshoot  
good phase margin ( $>65^\circ$ )
- Zero steady state error – very large DC gain

BODE PLOTS

#### METHOD

- Obtain linear small signal model
- Design controllers based on linear small signal model
- Perform large signal simulation for controllers verification

## CLOSED-LOOP SPEED CONTROL

### Closed-loop speed control – an example

Permanent magnet motor's parameters

$$R_a = 2 \Omega$$

$$L_a = 5.2 \text{ mH}$$

$$B = 1 \times 10^{-4} \text{ kg.m}^2/\text{sec}$$

$$J = 152 \times 10^{-6} \text{ kg.m}^2$$

$$k_e = 0.1 \text{ V}/(\text{rad/s})$$

$$k_t = 0.1 \text{ Nm/A}$$

$$V_d = 60 \text{ V}$$



$$V_{\text{tri}} = 5 \text{ V}$$

$$f_s = 33 \text{ kHz}$$

- PI controllers
- Switching signals from comparison of  $v_c$  and triangular waveform

# CLOSED-LOOP SPEED CONTROL

## Torque controller design

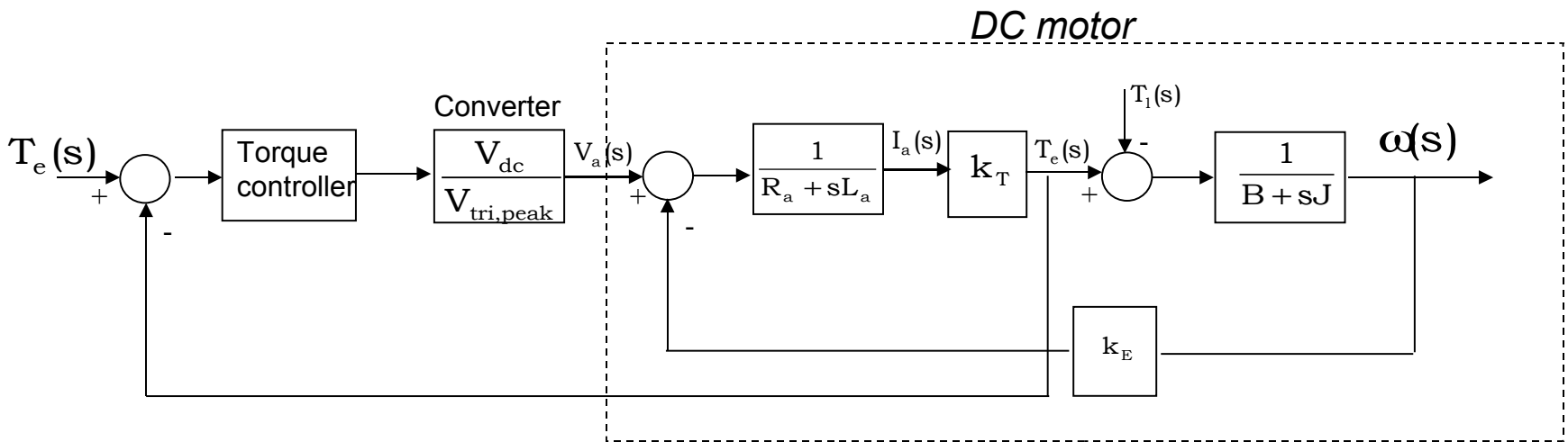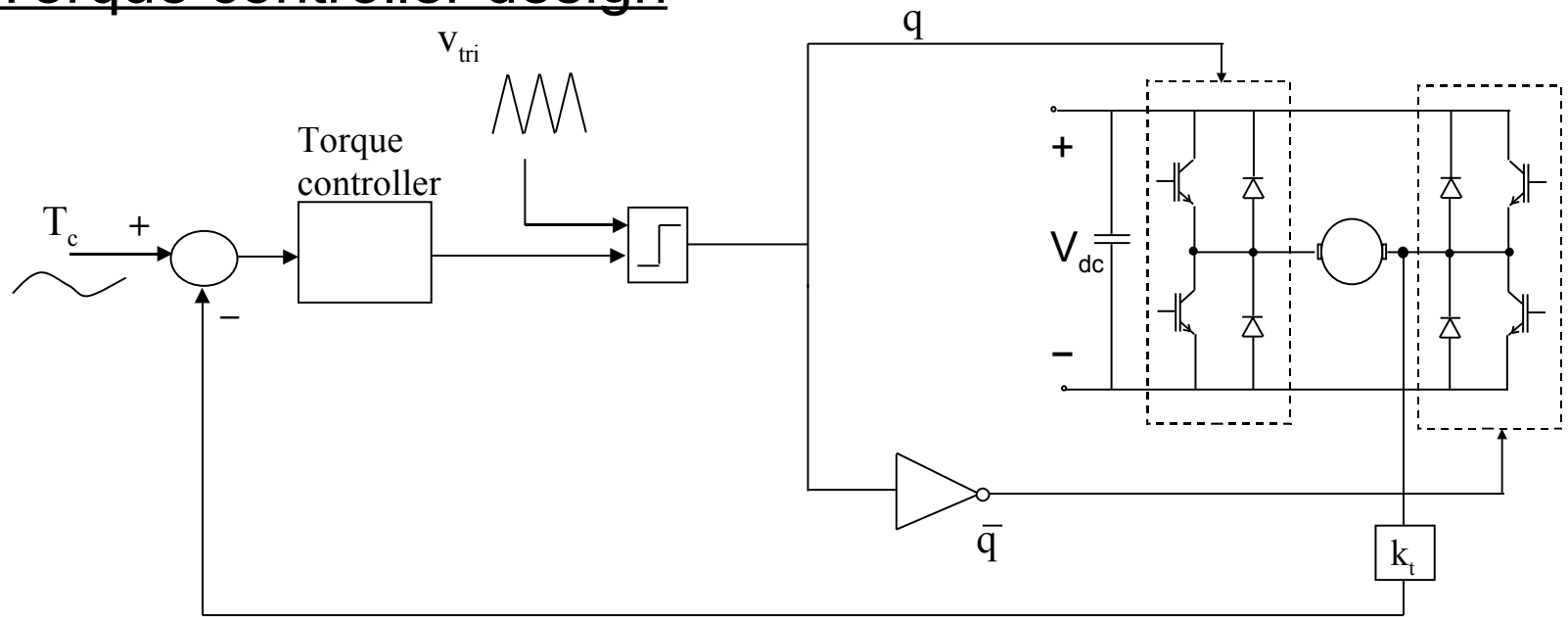




# CLOSED-LOOP SPEED CONTROL

## Torque controller design

*Open-loop gain*

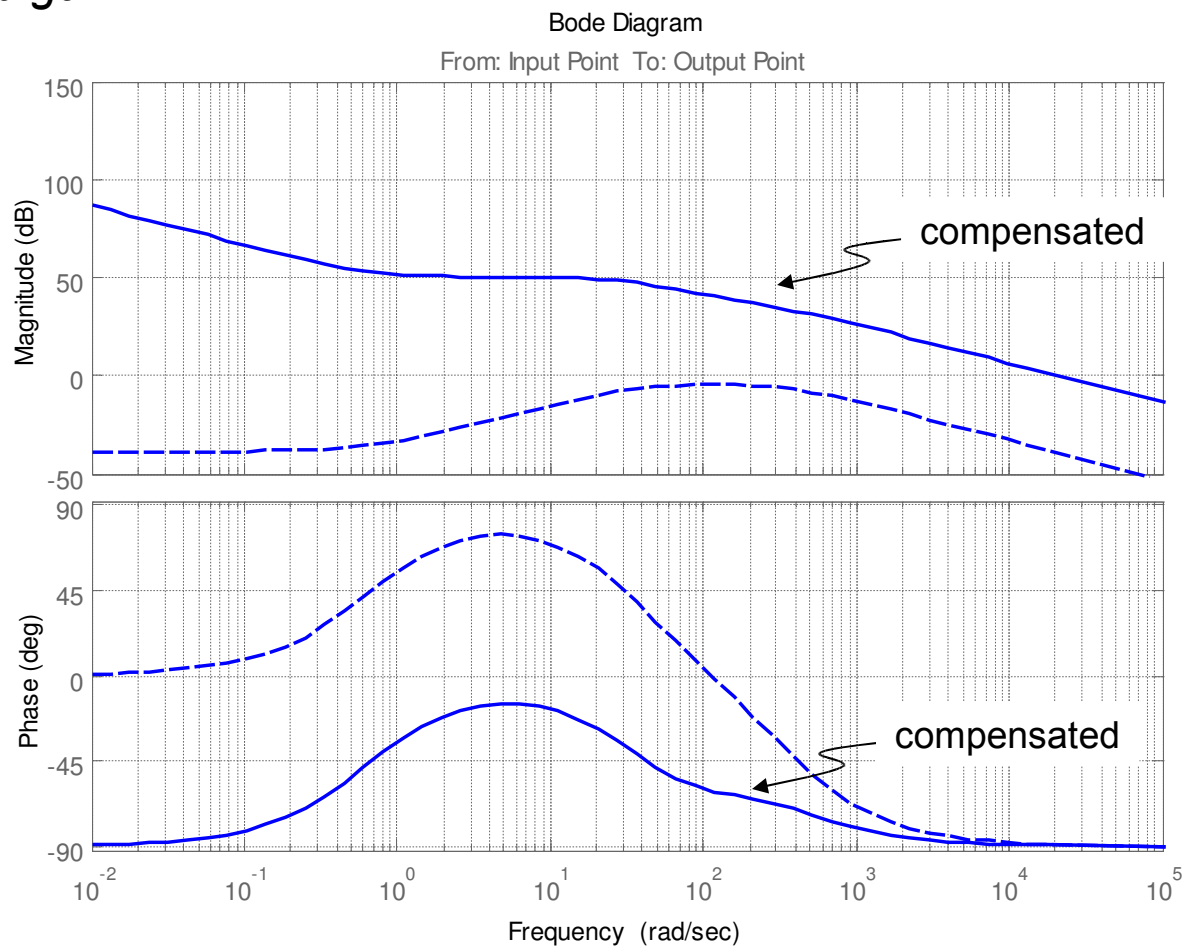


$$k_{pT} = 90$$

$$k_{iT} = 18000$$

## CLOSED-LOOP SPEED CONTROL
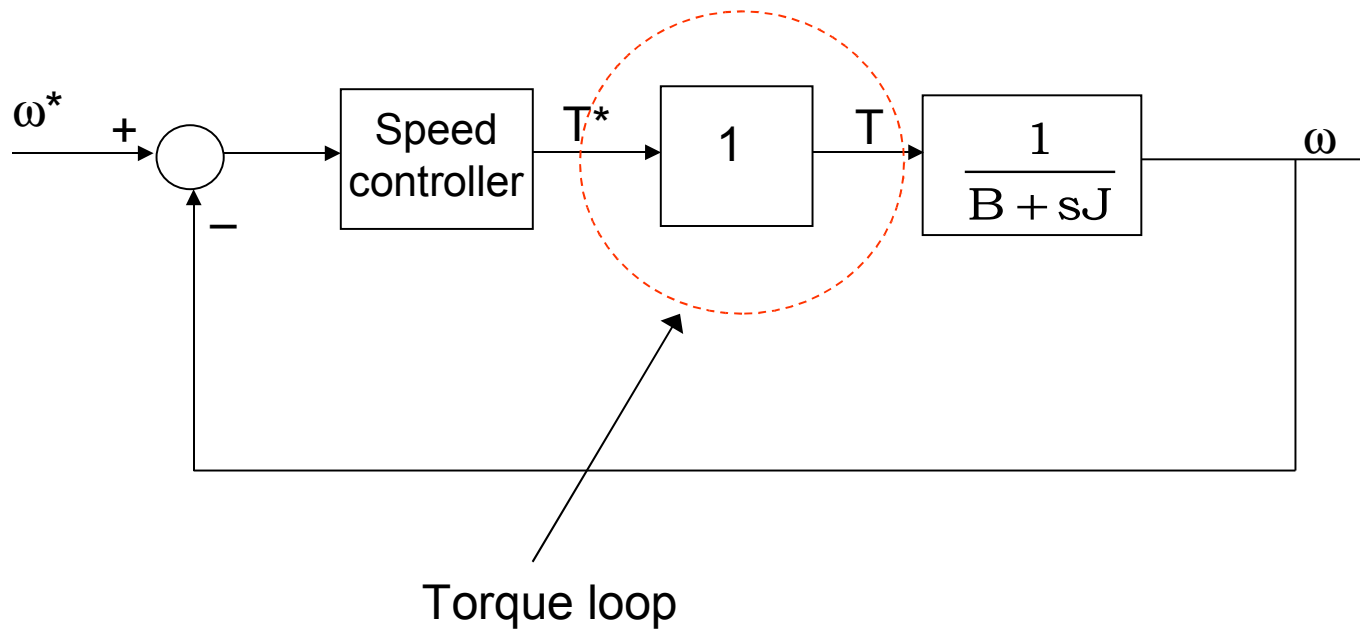
### Speed controller design


Assume torque loop unity gain for speed bandwidth  $\ll$  Torque bandwidth



# CLOSED-LOOP SPEED CONTROL

## Speed controller

*Open-loop gain*

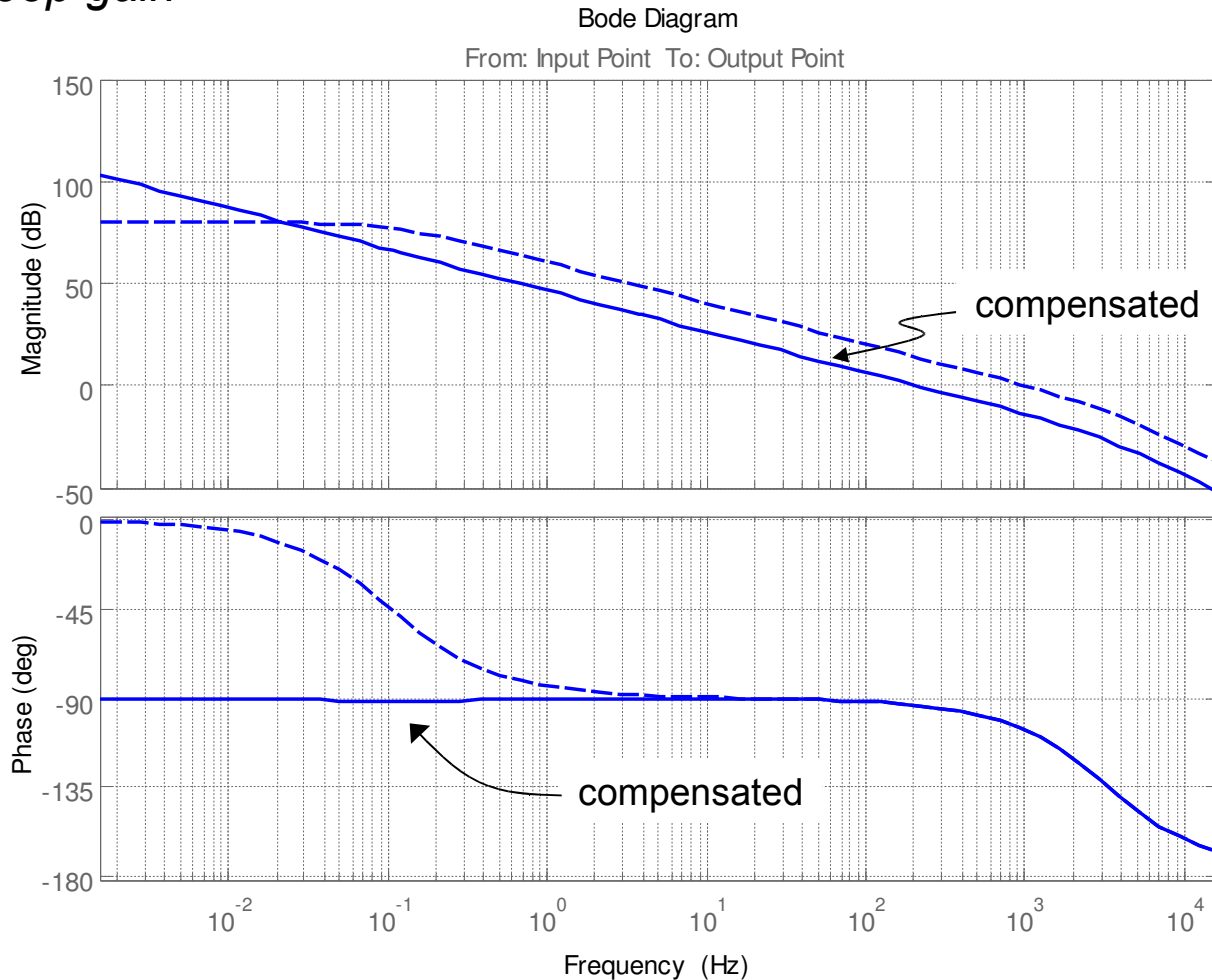


$$k_{ps} = 0.2$$

$$k_{is} = 0.14$$


# CLOSED-LOOP SPEED CONTROL

## Large Signal Simulation results

Speed

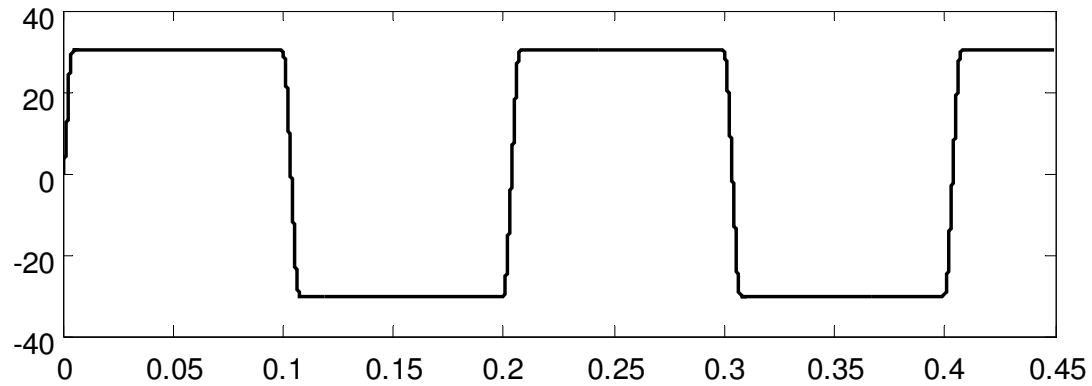

Torque

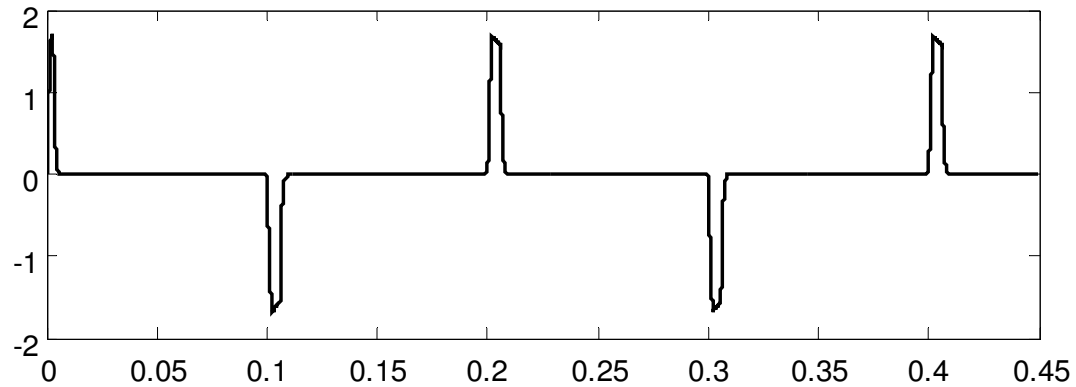

## CLOSED-LOOP SPEED CONTROL – DESIGN EXAMPLE

# SUMMARY

Speed control by: armature voltage ( $0 \rightarrow \omega_b$ ) and field flux ( $\omega_b \uparrow$ )

Power electronics converters – to obtain variable armature voltage

Phase controlled rectifier – small bandwidth – large ripple

Switch-mode DC-DC converter – large bandwidth – small ripple

Controller design based on linear small signal model

Power converters - averaged model

DC motor – separately excited or permanent magnet

Closed-loop speed control design based on Bode plots

Verify with large signal simulation